

## Short answer Q.

1. what is an electric circuit?
2. what do you mean by fused bulb?
3. what is open circuit?
4. what is close circuit?
5. Diff. between conductor and insulator.
6. what is electric switch.

DB: 09.02

Revision - 2

- ① Electric current flows only if the circuit is \_\_\_\_\_
- ② Electric wires are covered with \_\_\_\_\_
- ③ An electric bulb with a broken filament is \_\_\_\_\_  
Match

A

B

- |                                   |               |
|-----------------------------------|---------------|
| a. insulator                      | (i) copper    |
| b. make and break circuit         | (ii) Dry cell |
| c. Gas filled in an electric bulb | (iii) plastic |
| d. used in electric wires         | (iv) switch   |
| e. source of electric current     | (v) Argon     |